#### MIT ACADEMY OF ENGINEERING, Alandi (D)

(An Autonomous Institute Affiliated to Savitribai Phule Pune University)
School of Electrical Engineering

AY: 2020 - 2021

ET233 Microcontroller and Interfacing
PRACTICAL NO.--2
PIC 18F4520
a) LED's, Switch, Relay, Buzzer Interfacing and Embedded C Program
b) 7 segment Display

Savita Pawar

Write a program for interfacing switch, LED, relay & buzzer as follows

- A. when switch 1 is pressed relay and buzzer is turned OFF and LED's ON
- B. when switch 2 is pressed relay and buzzer is turned ON and LED'S OFF.
- C. Design & implement event counter using switch, Buzzer & 7segment Display


## Hardware Required

- PIC 18F4520 Microcontroller IC
- 8 LED's
- Reset Switch
- Resistors
- PORTD 8 pins
- + 5v supply & Ground

#### PIC 18F 4520 Pinout


2 3 4 5 6 7 14 13 35 36 37 38 39 40	RA0/AN0/C1IN- RA1/AN1/C2IN- RA2/AN2/C2IN+/VREF-/CVREI RA3/AN3/C1IN+/VREF+ RA4/T0CKI/C1OUT RA5/AN4/SS/HLVDIN/C2OUT RA6/OSC2/CLKO RA7/OSC1/CLKI  RB0/AN12/FLT0/INT0 RB1/AN10/INT1 RB2/AN8/INT2 RB3/AN9/CCP2A RB4/KBI0/AN11 RB5/KBI1/PGM RB6/KBI2/PGC RB7/KBI3/PGD	RC3/SCK/SCL RC4/SDI/SDA RC5/SDO RC6/TX/CK RC7/RX/DT RD0/PSP0 RD1/PSP1 RD2/PSP2 RD3/PSP3 RD4/PSP4 RD5/PSP5/P1B RD6/PSP6/P1C RD7/PSP7/P1D	15 16 17 18 23 24 25 26 19 20 21 22 27 28 29 30 8
		RE0/RD/AN5 RE1/WR/AN6 RE2/CS/AN7 RE3/MCLR/VPP	8 9 10 1


# Master Clear (Reset) pin

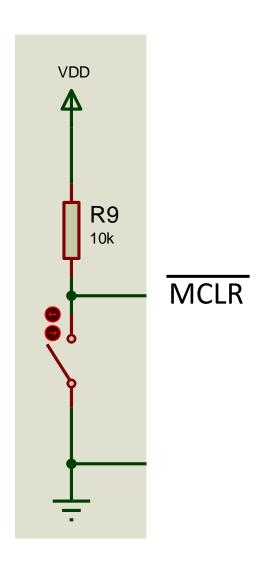


LED Connection


PIC 18F4520 Port pins

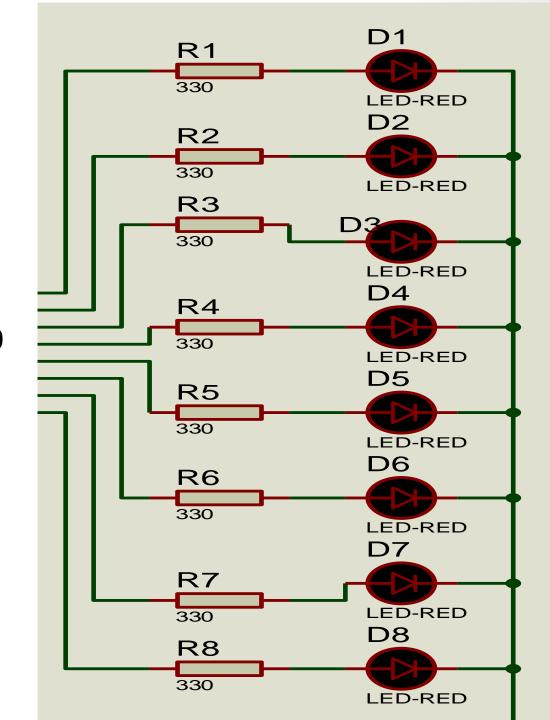

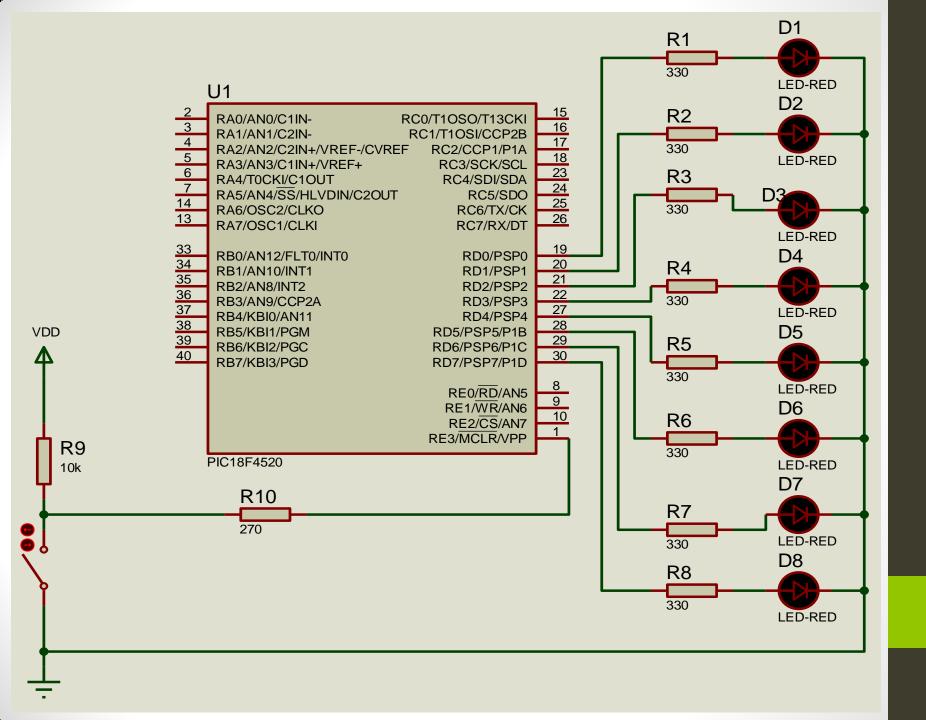

## Switch

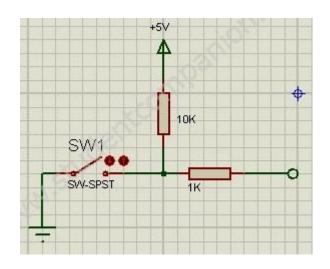


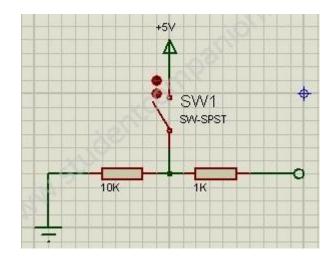


A Switch with a Pull-Up resistor

A Switch with a Pull-Down resistor


### Buzzer

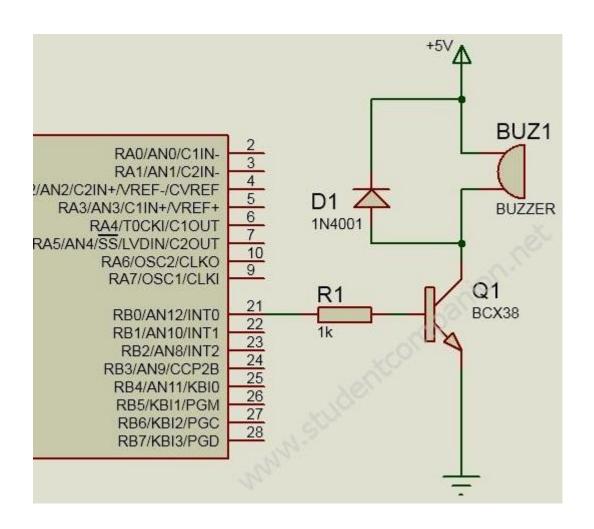

## Buzzer

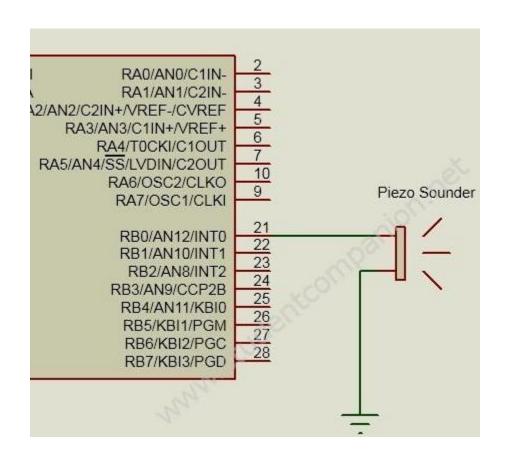

# Relay

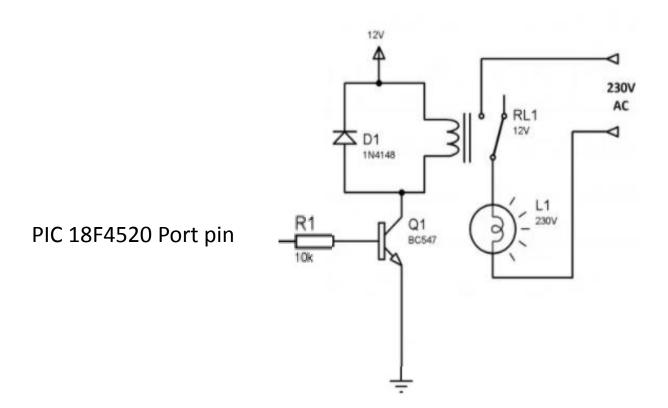

```
#include<PIC18F4520.h>
#pragma config OSC = HS
#pragma config PWRT=OFF
#pragma config WDT=OFF
#pragma config DEBUG=OFF, LVP=OFF
void msdelay(int a);
#define sw1 PORTBbits.RB7
#define sw2 PORTBbits.RB6
#define relay PORTCbits.RC7
#define buzzer PORTBbits.RBO
#define LED PORTD
```

```
// Initialization of PORT's in PIC
void main() {
  TRISD = 0;
  TRISC=0;
  TRISB= 0xC0;
  LED=0;
  relay=0;
  buzzer =0;
```

```
while(1)
    if(sw1==0 \& sw2==1)
      LED = OxFF;
      relay = 0;
                                if(sw1==1 \& sw2==0)
      buzzer=0;
                                        LED = 0;
      msdelay(1000);
                                        relay = 1;
                                        buzzer=1;
                                        msdelay(1000);
```

```
void msdelay(int a)
{
    for(int b=0;b<100;b++)
        for(int c=0;c<a;c++);
}</pre>
```

# 7 segment display


- Common Cathode (CC)
- Common Anode (CA)




7-segment Display

//www.electronics-tutorials.ws/blog

Reference

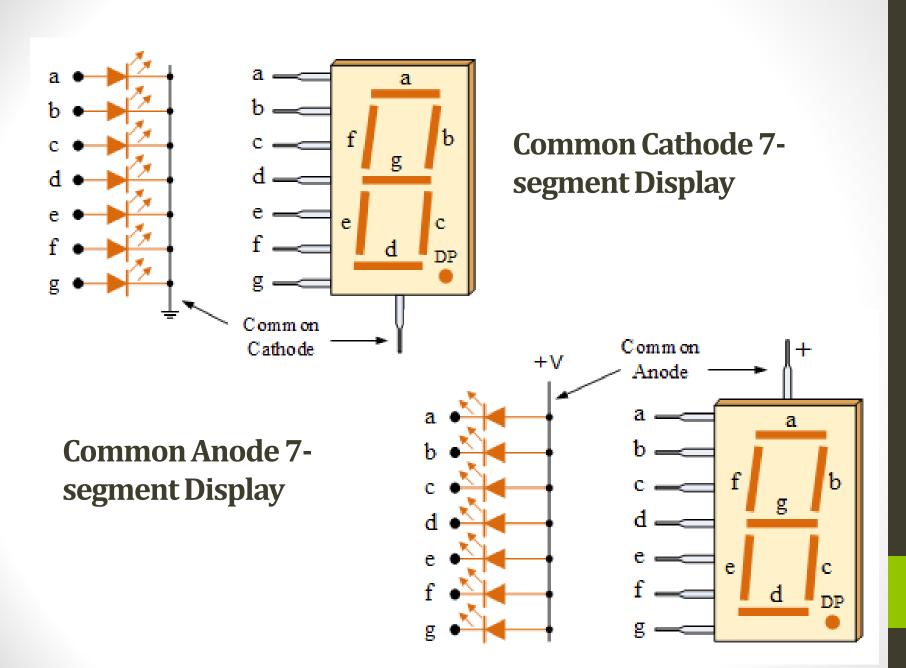

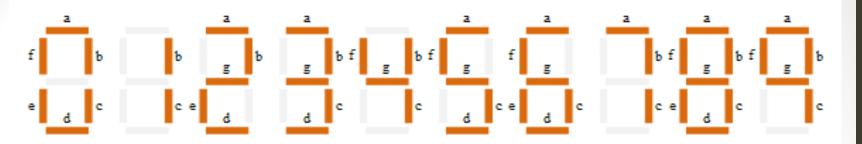
#### 7-Segment Display Segments for all Numbers



Number	ABCDEFG	PORTD (Hex)
0	00111111	0x3F
1	00000110	0x06
2	01011011	0x5B
3	01001111	0x4F
4	01100110	0x66
5	01101101	0x6D
6	01111101	0x7D
7	00000111	0x07
8	01111111	0x7F
9	01101111	0x6F
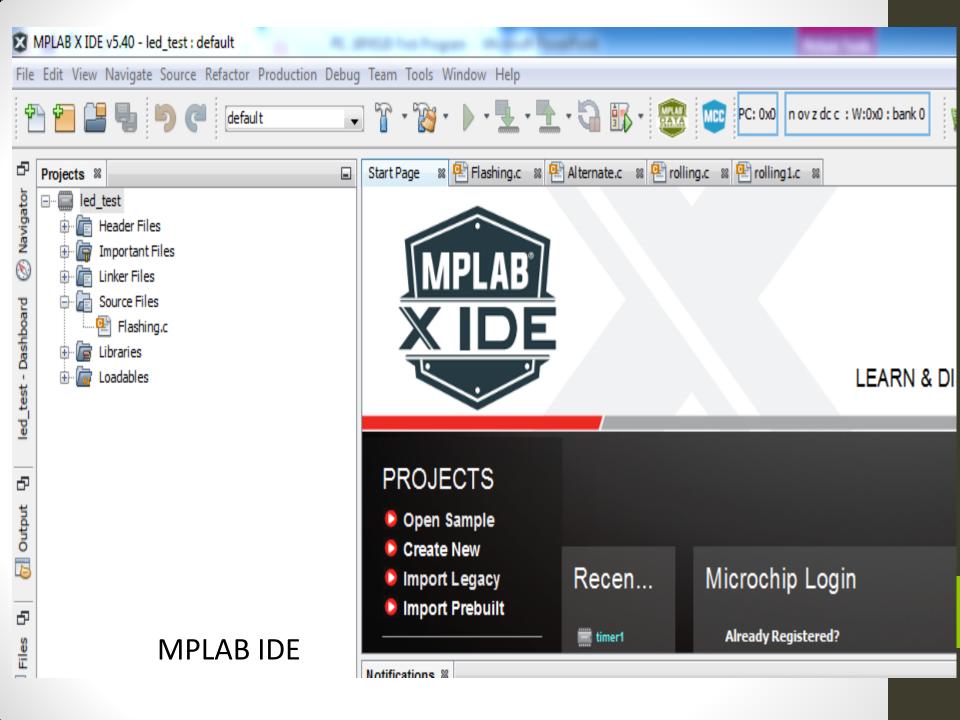
```
#include<PIC18F4520.h>
void msdelay(int a);
unsigned char binary pattern[] =
   {0x3F,0x06,0x5B,0x4F,0x66,0x6D,0x7D,0x07,0x7F,0x6F};
void main(void) {
  TRISD = 0x00; //define PORTD as a output pin
  while(1)
      for (int i=0;i<10;i++) {
      PORTD = binary_pattern[i];
      msdelay(1000); //add delay
  return;
```



# Thank you...



- Unsigned char a=00,b;
- For(a =0; a=<0xFF; a++)</li>
- b= a & 0x0F;
- PORTBbits.RB0 = 1;
- PORTBbits.RB1 = 0;
- PORTD= binary\_pattern[b];
- b = a & 0xF0;
- b = b >> 4;
- PORTBbits.RB1 = 1;
- PORTBbits.RB0 = 0;
- PORTD= binary\_pattern[b];